
NATCAR – Background Information

Pulsewidth Modulation (PWM) and DC Motors


Prof. Richard Spencer

Outline

- Pulse-Width Modulation (PWM)
- Comparator with Hysteresis
- Relaxation Oscillator
- The 555 Timer
- Review of basic electromagnetics
- DC motor operation & modeling

Pulsewidth Modulation (PWM)

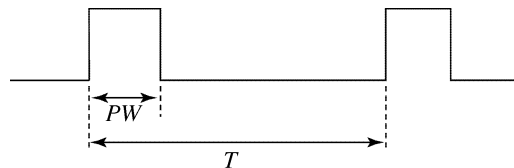
- A PWM signal is frequently used for transmitting information and for motor speed control.
- PWM signals are characterized by their period, T , which may or may not vary, their pulsewidth, PW , which does vary, and their voltage levels.



Comparator with Hysteresis - Circuit

To make a relaxation oscillator we need a comparator with hysteresis, as shown below.



This circuit can be made with an opamp:

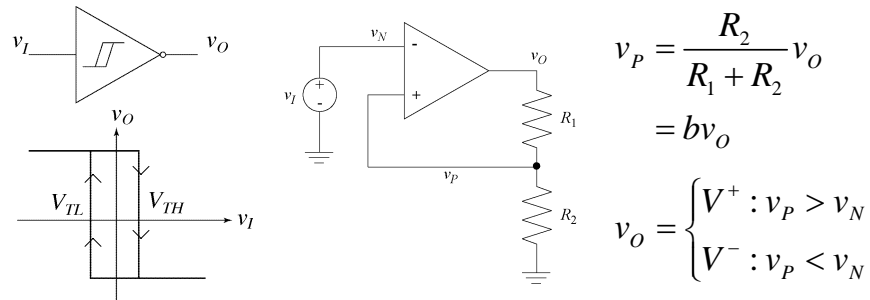

Comparator with hysteresis

Positive feedback produces hysteresis

Comparator with Hysteresis - Operation

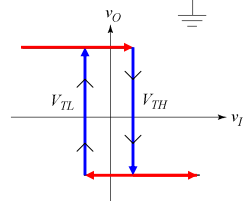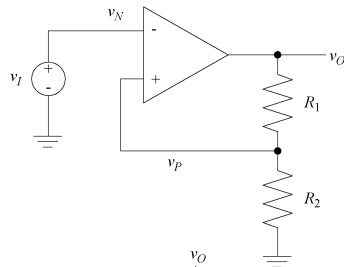

Comparator with hysteresis

To see the hysteresis in this circuit, start with v_O high (so $V_P = b v_O = V_{TH}$) and v_I low, then increase v_I .


When v_I reaches V_{TH} , the output goes low and V_P changes to V_{TL} .

Further increasing v_I doesn't change v_O .

Now reduce v_I ; this time, the threshold is at V_{TL} , and v_O goes high when v_I drops below V_{TL} .



Relaxation Oscillator

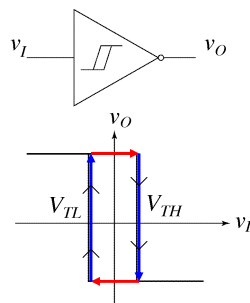The basic principle of a relaxation oscillator is shown here. A capacitor is alternately charged and discharged between two levels.



Comparator with hysteresis


Start at $t = 0^-$ with v_O low:

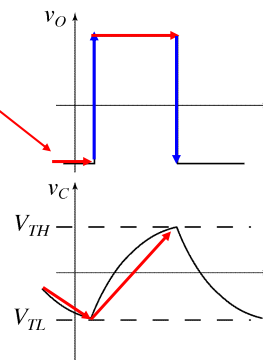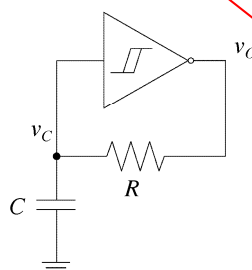


Relaxation oscillator

The 555 Timer

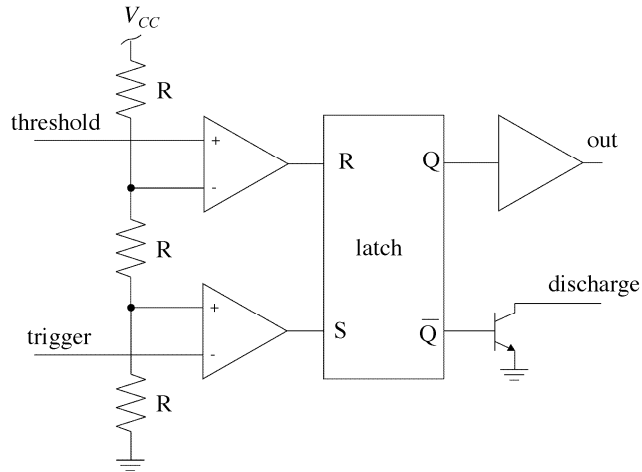
The 555 IC can be used to make an astable multivibrator (oscillator), a monostable (one-shot), a PW modulator and many other useful circuits.



Astable Oscillator with a 555

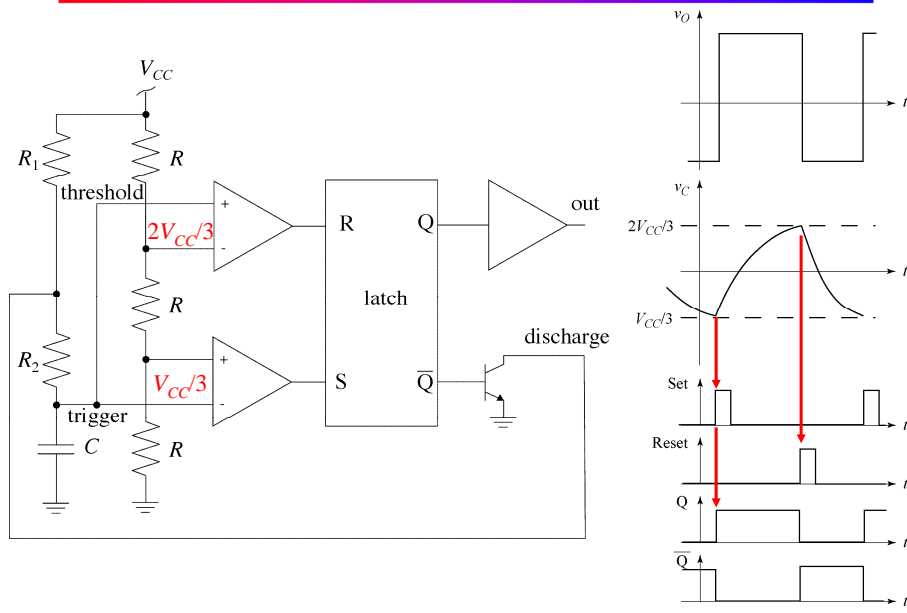

Astable Oscillator with a 555

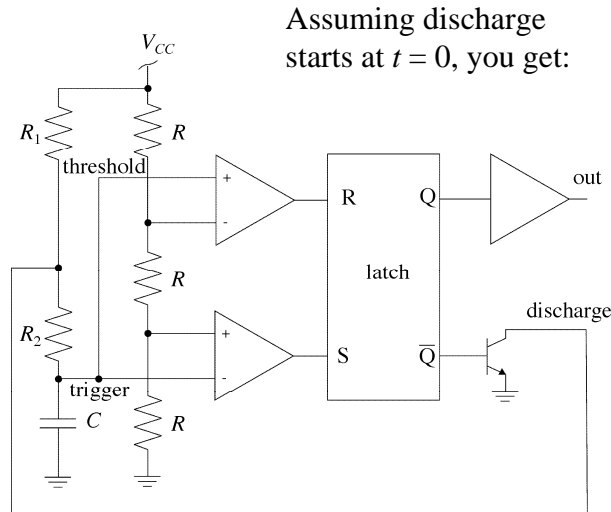

$$\frac{2V_{CC}}{3} e^{\frac{-t_L}{R_2 C}} = \frac{V_{CC}}{3}$$

$$t_L = -R_2 C \ln \frac{1}{2}$$

$$t_L = 0.7 R_2 C$$


You find t_H in the same way, so we get:

$$t_L = 0.7 R_2 C$$

$$t_H = 0.7 (R_1 + R_2) C$$

$$f = \frac{1}{T} = \frac{1}{0.7 (R_1 + 2R_2) C}$$

One-Shot with 555

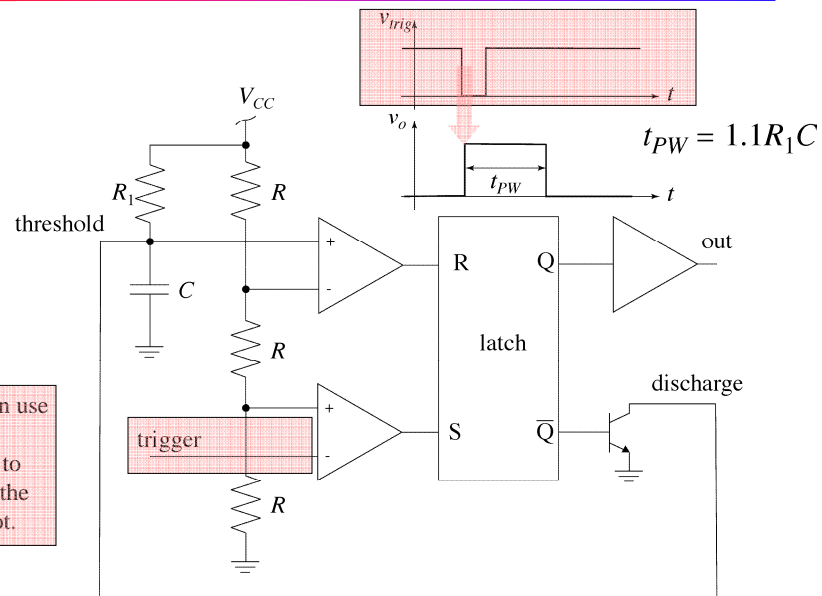

PWM with 555 Timer


- You can use the 555 one-shot circuit and vary the control voltage, the resistor, or the capacitor to change the pulse width.
- You can also build your own PWM circuit with a linear ramp and a variable threshold comparator. Custom PWM circuits may be more linear and have larger ranges.

PWM for the Steering Servo

- Standard radio-control (RC) car servos use a PWM control signal.
- You can drive them with a fixed or variable period PWM signal, all that matters is the pulse width and the voltage levels.
- Your servos can be supplied by a 5 or 6 volt supply (6 volts makes the servo faster, but > 6 volts will damage it).
- The PWM input signal is 0 to 5 volts. Typically, varying the *PW* from 0.5 ms to 2.5 ms causes the servo to turn lock-to-lock.

Basic Electromagnetics

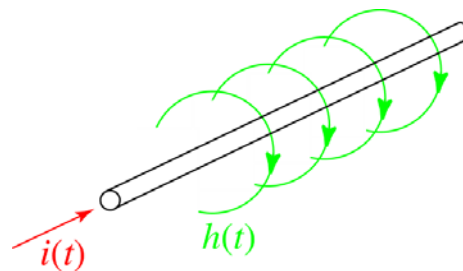- We will be dealing with motors and magnetic sensing. Therefore, we need to go over very basic electromagnetics.
- An electric current, I , produces a circular magnetic field with a magnetic field intensity, H , given by the law of Biot-Savart and the right-hand rule:



The diagram shows a horizontal wire with a red arrow labeled $i(t)$ pointing to the right, indicating the direction of current. Several green circular arrows are drawn around the wire, representing the circular magnetic field lines. One of these green arrows is labeled $h(t)$. To the right of the diagram is the Biot-Savart law equation:

$$dH = \frac{\vec{I} d\vec{L} \times \vec{a}_R}{4\pi R^2}$$


Electromagnetics Continued

- The magnetic field intensity is analogous to the electric field intensity, E . The magnetic flux, Φ , is analogous to the electric current, I , and the flux density, B , is analogous to current density, J . The flux density is $B = \mu H$, where μ is the permeability (similar to conductivity). The flux is $\Phi = B \cdot \text{area}$
- The electromotive force, emf , is given by Faraday's law and opposes the change that produced it: $emf = -d\Phi/dt$
- The Lorentz force on a charge is


$$\vec{F} = q(\vec{E} + \vec{v} \times \vec{B})$$

DC Motor Operation

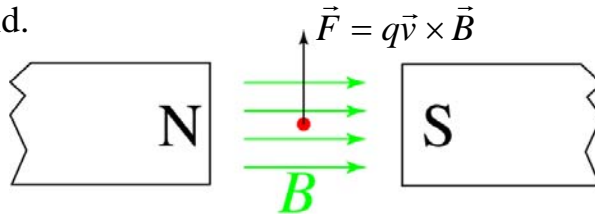- DC motors use the Lorentz force on a moving charge in a magnetic field. Assume no electric field.



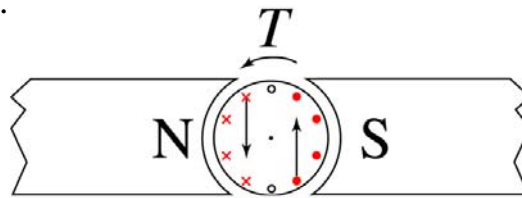- Multiple wires mounted on a rotor will produce torque.




DC Motor Construction

- The magnetic field can be produced by an electromagnet called the field winding, or by a permanent magnet. Our motors are permanent-magnet DC motors.
- Brushes are used to switch the current direction in the armature windings (see picture on next slide). This operation is called commutation.
- The torque produced is proportional to the current in the armature windings, I_A , and the magnetic flux, Φ :


$$T_m = k\Phi I_A$$

DC Motor Construction Continued

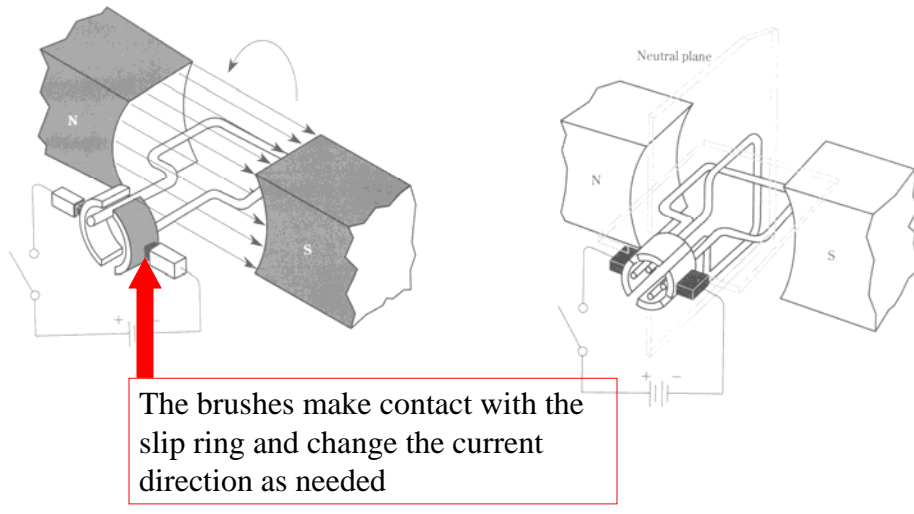

Permanent Magnet DC Motor

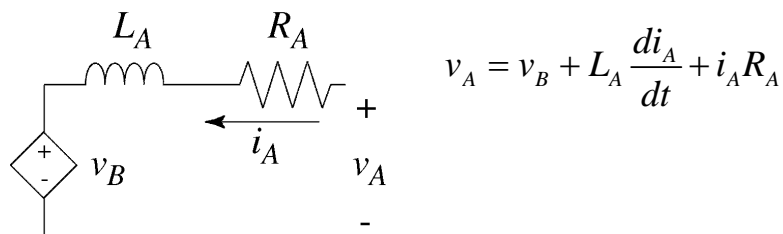- As the armature rotates, a back *emf* is produced that is proportional to the flux and the angular velocity. $v_B = k'\Phi\omega_m$
- The armature winding has resistance, inductance and the back *emf*, which leads to the electrical model shown:



Permanent Magnet DC Motor Continued

- Newton's second law in rotational form says that the product of the moment of inertia, J_m , and the rotational acceleration, equals the net torque;

$$J_m \cdot \frac{d\omega_m}{dt} = T_m - T_L - b\omega_m$$

where T_m is the motor torque, T_L is the load torque and b is the equivalent damping constant.

- In steady-state operation, the time derivatives are zero and we get

$$V_A = V_B + I_A R_A \quad \text{and} \quad T_m = T_L + b\omega_m$$

Remember we had: $T_m = k\Phi I_A$ and $v_B = k'\Phi \omega_m$

Permanent Magnet DC Motor Continued

Substitute for the current from the torque equation and use the equation we have for the back *emf* to get

$$V_A = V_B + I_A R_A = k'\Phi \Omega_M + \frac{R_A T_m}{k\Phi}$$

which can be rewritten as $\frac{\Omega_M}{\Omega_o} + \frac{T_M}{T_s} = 1$

where the no load speed is $\Omega_o = \frac{V_A}{k'\Phi}$

and the stall torque is $T_s = \frac{V_A k\Phi}{R_A}$

Motor Torque versus Speed

Note:

- That the current is largest when the speed and, therefore, the back *emf* are zero.
- That large stall torque is achieved with small armature resistance \Rightarrow high stall current.
- That both Ω_0 and T_S are proportional to V_A .

